

a.c

- (a) Define the following terms as applied to alternating Voltage.
- (i) Root – mean – square value,
 - (ii) Peak Value.(02)
- (b) (i) An alternating voltage is applied across a capacitor of capacitance, C .
show that the current in the circuit leads the voltage by $\frac{\pi}{2}$. (04)
- (ii) Find the expression for the capacitive reactance in terms of frequency, f and capacitance, C . (03)
- (iii) A capacitor of $0.1\mu\text{F}$ is in series with an a.c. source of frequency 500Hz . If the r.m.s value of the current flowing is 6mA , calculate the voltage across the capacitor.(03)
- iv) How a thermocouple can be used to measure a.c. (04)
- (c) A bulb is connected in series with an inductive coil and a d.c source as shown in Figure 3.


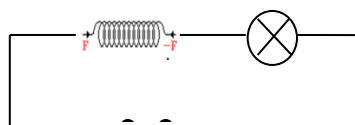


Figure 3

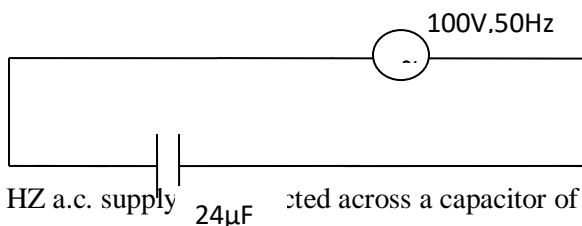- (i) What happens to the brightness of the bulb when an iron core is inserted in the coil? (01)
- (ii) Explain what happens to the brightness of the bulb when the d.c. source is replaced with an iron core inserted in the coil.(03)
- (d) How does an a.c transformer works. (05)
- 2 a) With the aid of a labeled diagram, describe how a repulsive to of moving iron ammeter works.(05)



- b) A 100V , 50Hz a.c. supply is connected across a capacitor of $24\mu\text{F}$ as shown in figure 3
- i) Calculate the reactance of the circuit (03)
 - ii) Sketch graphs to show the time dependence of the r.m.s voltage and the current in the circuit.(02)

- (c) An electric current flows through a coil of $4\ \Omega$ immersed in 200 g of water placed in a container. If the temperature of the water rises by 1K per minute, calculate the peak value of current supplied. (03 marks)
- (d) What is meant by **resonance** in a circuit? (01 mark)
- (e) A lamp of resistance $10\ \Omega$, a capacitor of capacitance $0.4\ \mu\text{F}$ and an inductor of inductance $0.4\ \text{H}$ are connected in series to an alternating voltage source of $0.01\ \text{V(r.m.s.)}$. The frequency f , is varied from low to high value while maintaining the amplitude of the applied voltage constant.
- (i) Explain how the brightness of the lamp varies. (03 marks)
 - (ii) Calculate the resonant frequency. (03 marks)
 - (iii) Find the voltage across the capacitor. (03 marks)
- (f) Explain why in an $R - C$ circuit, power is only absorbed by the resistive part of the circuit. (02 marks)